




#6




www.master-micro.com

Thursday Analog Quiz

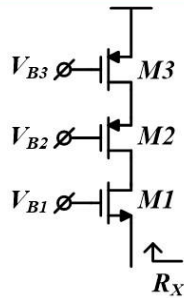


Assume M1, M2, and M3 have the same g_m and r_o , $g_m r_o \gg 1$, and neglect body effect. Find R_X .

we know that:

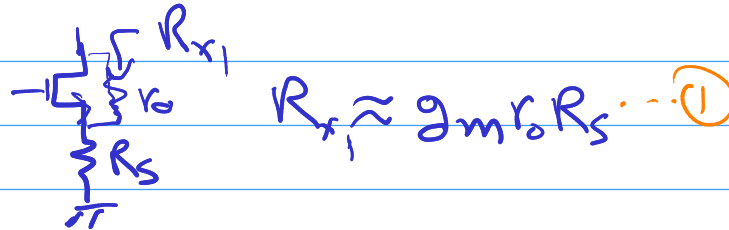

$$R_{X1} \approx g_m r_o R_S \dots (1)$$

and:

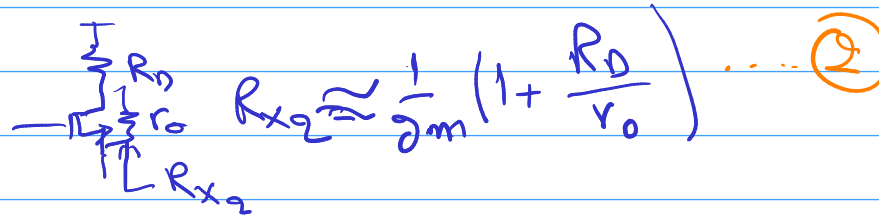

$$R_{X2} \approx \frac{1}{g_m} \left(1 + \frac{R_D}{r_o} \right) \dots (2)$$

using (1) and (2):

$$R_X = \frac{1}{g_m} \left(1 + \frac{R_{D1}}{r_o} \right) \text{ and } R_{D1} \approx g_m r_o^2$$

$$R_X = \frac{1}{g_m} \left(1 + \frac{g_m r_o^2}{r_o} \right) \approx r_o$$