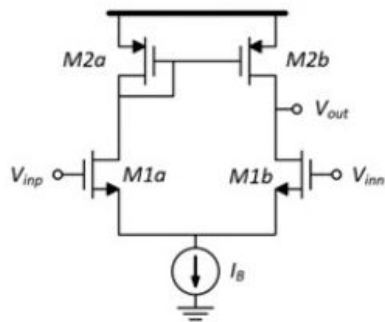


Consider the shown 5T OTA, and assume all devices are biased in weak inversion (WI) (Hint: In WI, the g_m/I_D almost saturates, and can be assumed constant). If the designer halved the bias current (I_B) (multiplied it by 0.5) and kept the sizing fixed, then:

- 1) The DC voltage gain is multiplied by
- 2) The bandwidth is multiplied by
- 3) The unity-gain frequency (UGF) is multiplied by
- 4) The input-referred noise density (in V^2/Hz) is multiplied by

Thursday Analog Quiz



This is not like Episode #3!

as we are in WI, g_m will change linearly with I_D
so

$$g_m = \frac{2I_D}{V_D}$$

$$g_m \times \frac{1}{2}$$

1) A_V :

$$r_o = \frac{1}{\lambda I_D} \Rightarrow r_o \times 2$$

$$A_V = G_m R_{out}$$

$$\text{and } G_m = g_m, R_{out} = r_{o1} \parallel r_{o2}$$

$$A_V \times 1$$

2) Bandwidth:

$$BW = \frac{1}{2\pi R_{out} C_{out}} \Rightarrow BW \times \frac{1}{2}$$

3) Unity Gain frequency:

$$UGF = GBW = A_V \cdot BW \Rightarrow UGF \times \frac{1}{2}$$

4) Input-referred noise density $\overline{v_n^2}$:

$$\overline{v_n^2} \propto \frac{1}{g_m} \Rightarrow \overline{v_n^2} \times 2$$

Comparison btw SI and WI:

when halving the bias current: (when fixing sizing)

	WI	SI	comments
g_m	linear with I_D $\times 0,5$	degrade less $\times 0,707$	SI
g_m / I_D	constant $g_m / I_D = \frac{1}{n V_T}$	$\times 1,414$	
A_v	constant	$\times 1,414$	in SI we get gain boost
UGF	$\times 0,5$	$\times 0,707$	in WI we get slower
BW	$\times 0,5$	$\times 0,5$	
$\overline{V_n^2}$	$\times 2$	$\times 1,414$	In WI we get harsher in noise