

MASTER ICR
Your one-stop shop for Mastering Microelectronics


ADT
Analog Designer's Toolbox
From Designers... To Designers

#9



adt.master-micro.com

Thursday Analog Quiz

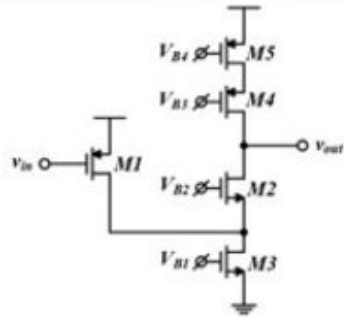

All transistors are biased at $g_m/I_D = 10 \text{ S/A}$ and have early voltage $V_A = 10 \text{ V}$. Assume $g_m \cdot r_o \gg 1$ and neglect body effect. Calculate $A_v = G_m \cdot R_{out}$.

$$A_v = G_m R_{out}$$

$$G_m = g_{m1}$$

$$R_{out} = g_{m1} r_{o1} r_{o5} // g_{m2} r_{o2} (r_{o3} // r_{o1})$$

Q3 M_3 carry double the current of M_1 so $g_{m3} = 2g_{m1}$

$$r_{o3} = \frac{r_{o1}}{2} \Rightarrow R_{out} = g_{m1} r_o^2 // g_{m1} r_o \left(\frac{r_{o1}}{3} \right) = g_{m1} r_o^2 // \frac{g_{m1} r_o^2}{3}$$

$$R_{out} = \frac{\frac{g_{m1} r_o^4}{3}}{4 g_{m1} r_o^2} = \frac{g_{m1} r_o^2}{4 g_{m1} r_o^2} = \frac{g_{m1} r_o^2}{4}$$

$$A_v = G_m R_{out} = (g_{m1} r_o^2) \frac{1}{4} = \frac{1}{4} \left(g_{m1} \frac{V_A}{I_D} \right)^2$$

$$A_v = \frac{1}{4} \left(\frac{g_{m1}}{I_D} \cdot V_A \right)^2 = 2500$$