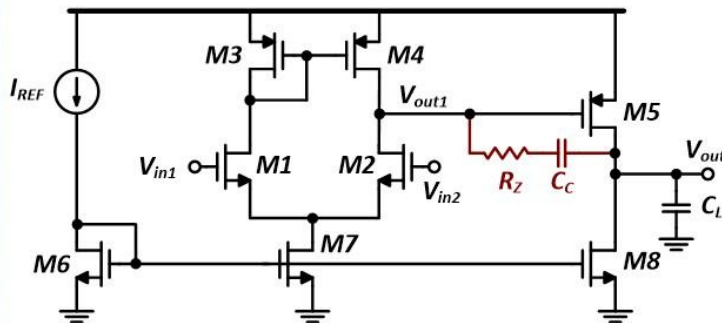




Thursday Analog Quiz



If we want to use this OTA as a unity gain buffer, what connection should be made? Where should the input signal go?

to configure the opamp as unity-Gain buffer, we need to link the output to the inverting terminal V_{in1} while, while linking the input signal to V_{in2} .