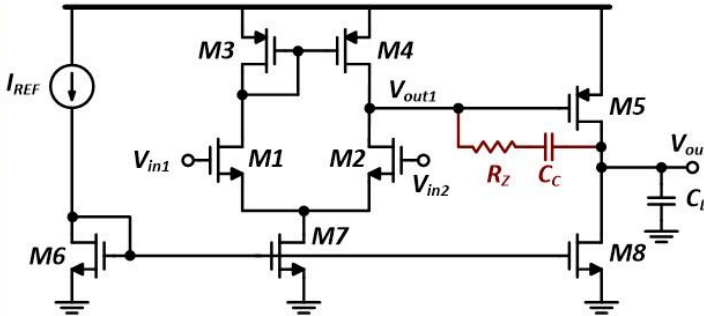




Thursday Analog Quiz



Assume all transistors are biased in SI and the square-law is valid. If IREF is halved (x 0.5), the DC gain is multiplied by how much?

gain of stage 1: A_{V1}

gain of stage 2: A_{V2}

$$A_{V_{total}} = A_{V1} \cdot A_{V2}$$

$$A_{V1} = g_{m2} \cdot R_{out1}$$

$$\frac{I_{REF}}{2} \Rightarrow I_2 = \frac{I_{REF}}{2} \times \frac{1}{2} \Rightarrow I_2 \times \frac{1}{2}$$

$$g_m = \sqrt{2I_D \frac{W}{L} V_{OV}} \Rightarrow g_m \times \frac{1}{\sqrt{2}}$$

$$R_{out} \times 2 \quad \text{as} \quad r_o = \frac{1}{\lambda I_D}$$

$$A_{V1} \times \frac{2}{\sqrt{2}}$$

$$A_2 = g_{m5} R_{out2}$$

$$I_5 = I_{REF} \Rightarrow I_{REF} \times \frac{1}{2} \Rightarrow I_5 \times \frac{1}{2}$$

$$g_{m5} \times \frac{1}{\sqrt{2}} \quad \text{and} \quad R_{out2} \times 2 \Rightarrow$$

$$A_{V2} \times \frac{2}{\sqrt{2}}$$

$$A_V \times \frac{2}{\sqrt{2}} \times \frac{2}{\sqrt{2}} \Rightarrow A_{V_{total}} \times 2$$