


MASTER ICR
Your one-stop shop for Mastering Microelectronics


ADT
Analog Designer's Toolbox
From Designers... To Designers

#10




adt.master-micro.com

Thursday Analog Quiz

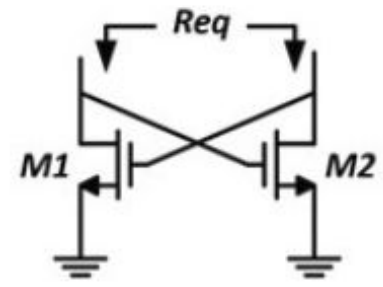

Assume $g_m \cdot r_o \gg 1$. Derive an expression for R_{eq} . Can you mention two different types of circuits that use this cross-coupled structure?

We apply a test voltage:

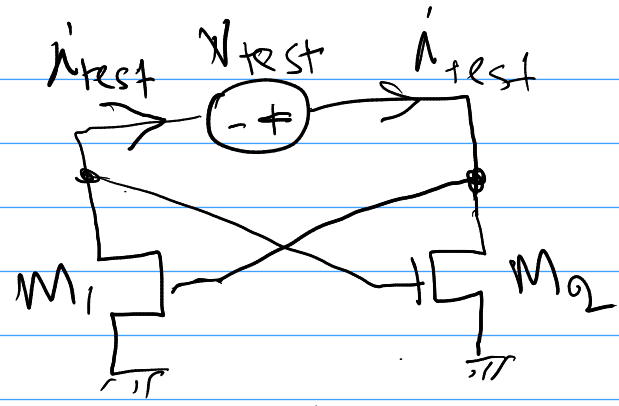

$$i_{test} = g_m V_{GS2} + \frac{V_{GS1}}{r_o} \quad \text{--- (1)}$$

$$i_{test} = - \left(g_m V_{GS1} + \frac{V_{GS2}}{r_o} \right) \quad \text{--- (2)}$$

(1) + (2):

$$2 i_{test} = (V_{GS2} - V_{GS1}) g_m + \left(\frac{V_{GS1} - V_{GS2}}{r_o} \right) \text{ as } V_{test} = V_{GS1} - V_{GS2}$$

$$2 i_{test} = - V_{test} g_m + \frac{V_{test}}{r_o}$$

$$2 i_{test} = V_{test} \left(\frac{1 - g_m r_o}{r_o} \right)$$

$$\frac{V_{test}}{i_{test}} = - \frac{2}{g_m}$$

this circuit has a characteristic of positive feedback.
and it's used in latched comparators.