

ADT
Analog Designer's Toolbox
From Designers... To Designers

#1

adt.master-micro.com

For the shown differential amplifier, assume $g_m \cdot r_o \gg 1$ and ignore body effect. Assume M1 has $g_m/I_D = 16$ and M2 has $g_m/I_D = 8$.

- 1) The DC voltage gain is equal to
- 2) If the square-law is valid and $L_1 = L_2$, then $W_1/W_2 = \dots$

1) DC gain:

first we need to find resistance at output node, assuming $r_{o1} = r_{o2} = r_o$

$$R_{out} = r_o \parallel r_o \parallel \frac{1}{g_{m1}}$$

$$R_{out} = \frac{r_o}{2g_{m1} + 1/r_o}$$

as $g_m r_o \gg 1$:

$$R_{out} = \frac{1}{2g_{m1}}$$

so the gain is:

$$A_v = \frac{2g_{m1}}{2g_{m1}} = 1$$

as M_1 and M_2 both of them flow a current of $I_B/2$ on them and $\left(\frac{2g_m}{I_{D1}}\right) = 16$, $\left(\frac{2g_m}{I_{D2}}\right) = 8$

$$\text{so } \Rightarrow g_{m1} = \frac{64}{I_B}, \quad g_{m2} = \frac{32}{I_B}$$

resulting in a gain:

$$A_v = \frac{64}{32} = 2$$

2) same $L \Rightarrow$ same r_o ($I_{D1} = I_{D2}$)

using this g_m equation:

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}, \quad L_1 = L_2$$

$$\frac{g_{m1}}{g_{m2}} = \sqrt{\frac{W_1}{W_2}} \Rightarrow \sqrt{\frac{W_1}{W_2}} = 2 \Rightarrow \frac{W_1}{W_2} = 4$$